
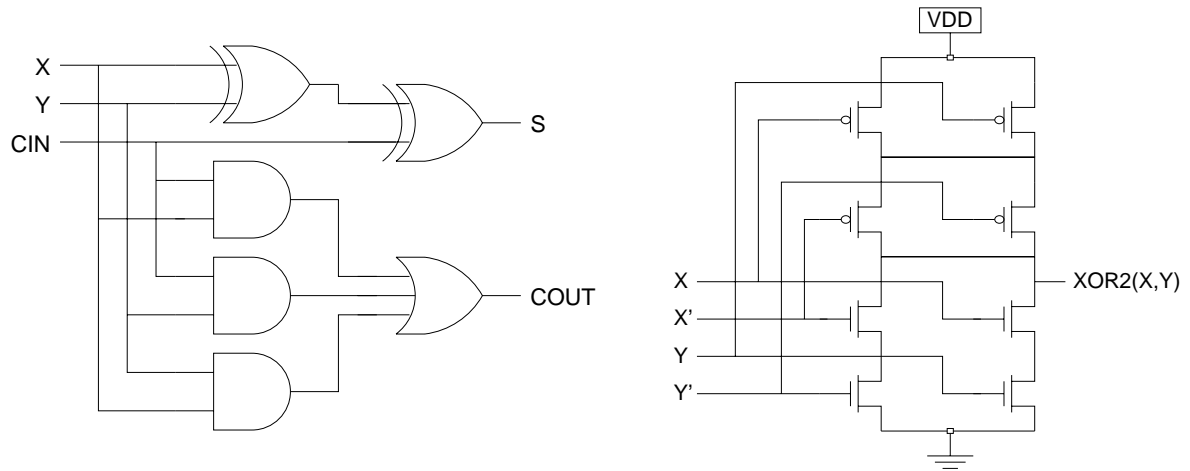


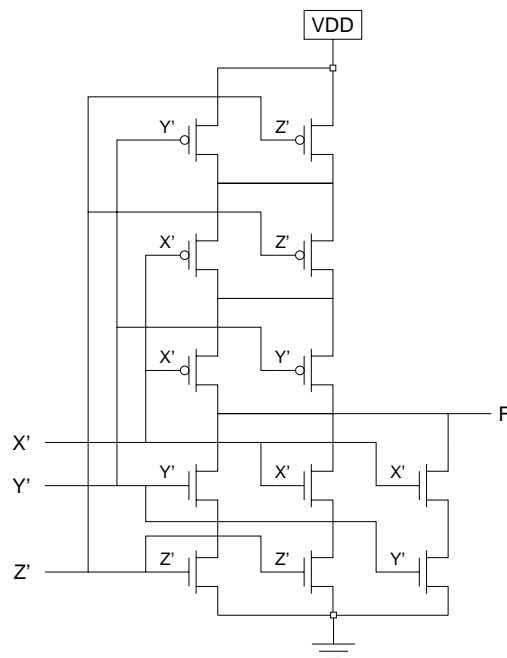2. (20 points) *Full adder CMOS logic circuit.* A gate-level circuit diagram for a full adder and a CMOS logic circuit for an XOR gate are shown below. The XOR can be built with only 8 transistors, provided the complements of the inputs are available. (For this problem, it is *not* necessary to understand how the XOR circuit works.)






Since the complements of the inputs are needed for the XOR circuit, it makes sense to use them elsewhere in a CMOS logic circuit for a full adder. Design a CMOS logic circuit using 12 transistors (6 p-channel and 6 n-channel) that computes COUT from the complements X' , Y' , CIN' of the input signals. Hint: $\text{majority}(X, Y, Z) = \text{minority}(X', Y', Z')$.



The output F is connected to ground through a series connection of two n-channel transistors if any two of X' , Y' , or Z' are true. Otherwise, if at least two of X, Y, or Z are true, F is connected to VDD through at least one path. Thus F is the majority function. It is easy to eliminate two transistors by merging the pairs of transistors with input X' .

 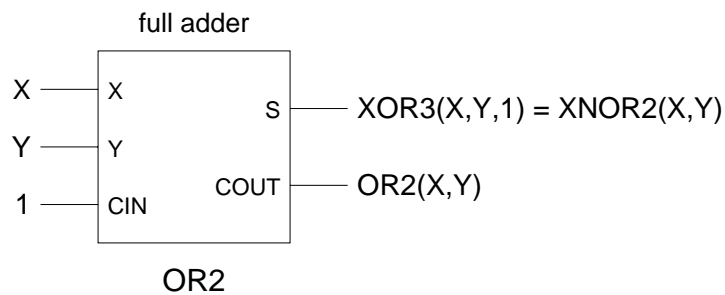 3. (20 points) *Full adders are complete.* Full adders form a *complete* set of logic gates; that is, every Boolean function can be implemented using only full adders.



- a. Wire each of the full adders above to produce the specified logic function (AND2, OR2, or NOT). In each case, only one output of the full adder is used. The full adder inputs may be connected to primary input signals or to constant values 0 or 1.
- b. In each case, the “unused” output of the full adder is a Boolean function. Write next to that output pin the name or formula for this bonus output.