

Midterm Examination #2

Open book, open notes. Time limit: 2 hours

Honor Code Acceptance: This examination has been written according to the spirit and principles of the Stanford Honor Code.

Signature

Print Name

Problem	Score
#1	/ 12
#2	/ 13
#3	/ 20
#4	/ 20
#5	/ 10
#6	/ 25
Total	/ 100

Midterm Examination #2

Open book, open notes. Time limit: 2 hours

1. (12 points) *Multiplication*. The unsigned product of 2-bit numbers A_1A_0 and B_1B_0 is a 4-bit result $Y_3Y_2Y_1Y_0$. For example,

$$11_2 \cdot 11_2 = 3_{10} \cdot 3_{10} = 9_{10} = 1001_2.$$

Find efficient Boolean formulas for the product bits $Y_3Y_2Y_1Y_0$ as functions of the bits of the multiplier A_1A_0 and the multiplicand B_1B_0 .

$Y_0 =$ _____

$Y_1 =$ _____

$Y_2 =$ _____


$Y_3 =$ _____

Hint: the formulas for Y_0 and Y_3 are *very* simple. Remark: the best equations are *not* the minimal sums of products.

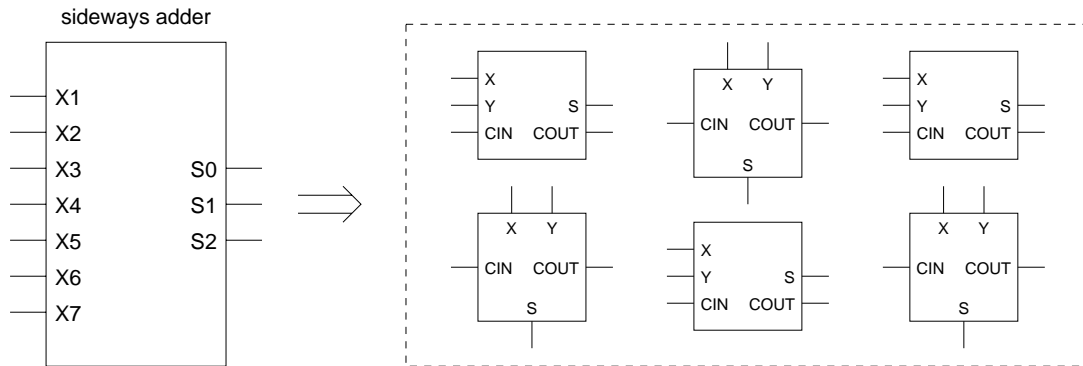2. (13 points) *Sideways adder*. The *sideways sum* of a signal vector (X_1, X_2, \dots, X_n) is the number of input signals that are true; that is,

$$S = \sum_{k=1}^n X_k.$$


Since S has $n + 1$ possible values, the sum requires a vector of $m = \lceil \log_2(n + 1) \rceil$ bits. For $n = 7$, the sum is represented by $\lceil \log_2(7 + 1) \rceil = \lceil \log_2 8 \rceil = 3$ bits; that is, $S = (S_2, S_1, S_0)$.



Using only full adders, design a circuit that calculates the sideways sum (S_2, S_1, S_0) of (X_1, X_2, \dots, X_7) . You may use either of the two alternative logic symbols for the full adder. (Do not try to wire the full adders inside the box above.) Hint: six full adders are more than enough. Bonus points for minimum number of gates and smallest propagation delay.

3. (20 points) *Latches?*

 - a. A committee of logic designers could not agree on whether to use NAND gates or NOR gates to build a set-reset latch. The compromise design is shown below.




Fill in the function table for this sequential circuit.

X	Y	Q	/Q
0	0		
0	1		
1	0		
1	1		


Explain what is wrong with this “latch”?

 - b. The feedback sequential circuit shown below is intended to change state with each clock pulse; in other words, it is supposed to be a “toggle latch.”



Explain why this sequential circuit does not work as intended. What actually happens?

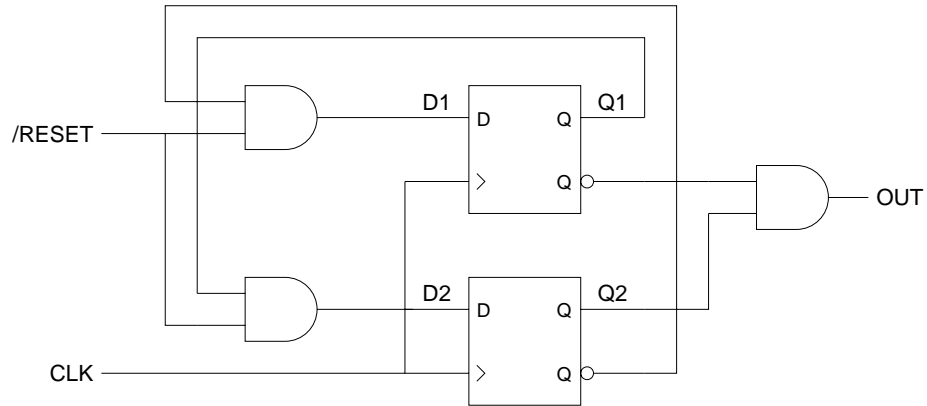4. (20 points) *State machine analysis.* Analyze the clocked synchronous state machine below.



a. Draw a state diagram for this state machine.


b. Is this machine a Mealy machine or a Moore machine?

Answer (circle one): Mealy Moore

c. Fill in the transition/output table for the above state machine.

		/RESET		
Q1	Q2	0	1	OUT
0	0			
0	1			
1	0			
1	1			
		Q1*Q2*		

 5. (10 points) A negative edge-triggered D flip-flop can be built from a positive edge-triggered D flip-flop and an inverter, as shown below.



The propagation delays and timing parameters for the inverter and the D flip-flop are given in the following tables.

Inverter		
	min	max
t_{pLH}	5	7
t_{pHL}	3	5


Flip-Flop	
t_s	6
t_h	2

Find the setup time t_s and the hold time t_h for this negative edge-triggered flip-flop.

Setup time $t_s =$ _____

Hold time $t_h =$ _____

 6. (25 points) *Variable-speed counter*. The 24-bit binary counter shown below counts either at full speed or at half speed as determined by the speed-control state machine **SPEED**.



In half-speed mode, **SPEED** enables counting on every other clock, whereas in full-speed mode, the counter enable **CE** is always true. The speed is changed by the pushbutton input **BIN**; each positive pulse of **BIN** toggles the speed mode, from half to full or from full to half. This input is debounced, and its pulse width is a large number of clock cycles.

- a. Draw the state diagram for the **SPEED** state machine.

b. For a state assignment of your choice, write the transition/output table.

c. For the state assignment of part b, write the transition and output equations.