

Administrative issues

- Midterm #1 will be given Tuesday, October 29, at 9:30am.
 - The entire class period (75 minutes) will be used.
 - Open book, open notes.
 - *DDPP* sections: 2.1–2.6, 2.10–2.13, 3.1–3.4, 3.7, 4.1–4.3.7, 4.5, 5.1–5.2, 5.4–5.5, 5.7, 5.9, 6.1.
- Lab #5 will be handed out next week and due November 6–7.

No laboratory assignment next week. :-)

Sequential logic

Executive summary of EE 121: combinational logic easy, sequential logic hard.

Combinational logic = truth tables.

Combinational logic synthesis can be greatly aided by clever decomposition of the problem. Example: 8-bit adder built using two 4-bit adders.

Sequential logic = simple matter of programming. ;-)

Designing state machines is similar to programming, but much harder because things happen in parallel.

In software programs, data is stored in *variables*—simple state machines that remember one or more bits. A stored value remains unchanged until a new value is loaded. The values of the variables are *part* of the state of the system.

State machine examples

“Complex” state machines:

- Record/play control for digital audio (EE 121 lab #6)
- Control unit for computer (very ambitious final project)

Examples of small state machines:

- Light switch controller (toggle on/off)
- Simultaneous button push detector
- Push button processor converts long button push to one clock cycle pulse

What these examples have in common: the output is a function of past inputs (memory) as well as current input.

State machines

A state machine is a sequential circuit whose outputs depend on the current state (values of memory devices) and whose state changes based on current state and inputs.


$$\begin{aligned} \text{state} &= F(\text{state}, \text{input}) \text{ — next state function} \\ \text{output} &= G(\text{state}, \text{input}) \text{ — output function (may not depend on input)} \end{aligned}$$

State machines may be asynchronous or synchronous:

- State transitions may occur at any time when input changes
Examples: R-S latch, D latch
- State transitions occur only at times determined by system clock, usually at active an clock edge.
Examples: D flip-flop, shift register = series of D flip-flops

Clocked synchronous state machines: Mealy

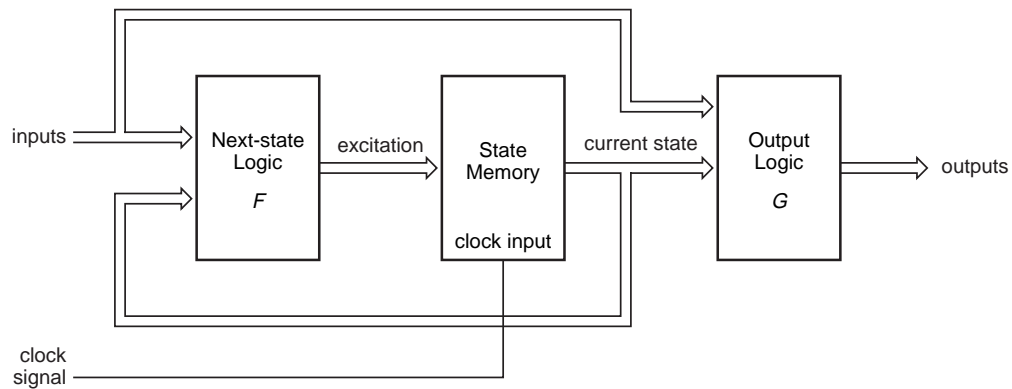Mealy machine: output depends on state and current input.



George Mealy worked at Bell Labs in the 1950s.


October 22, 2002

EE 121: Digital Design Laboratory

Lecture 8-5

Clocked synchronous state machines: Moore

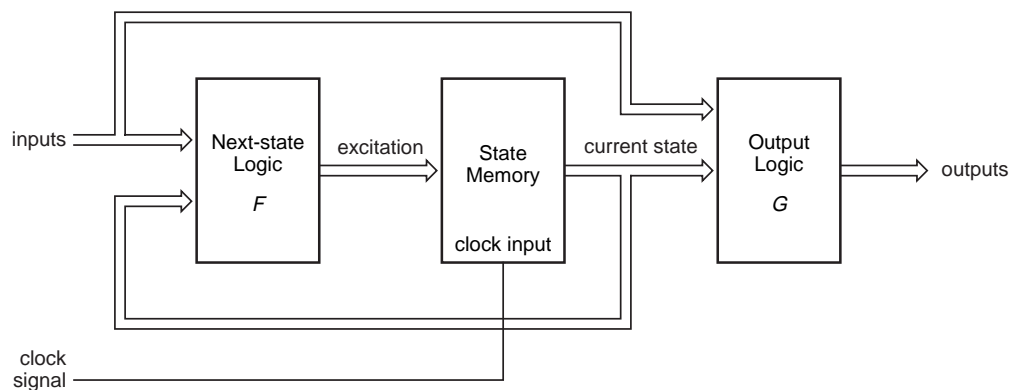Moore machine: output depends only on current state.



E.F. Moore was Electrical Engineering professor at the University of Pennsylvania after working at Bell Labs.


October 22, 2002

EE 121: Digital Design Laboratory


Lecture 8-6

Mealy vs. Moore

Mealy:

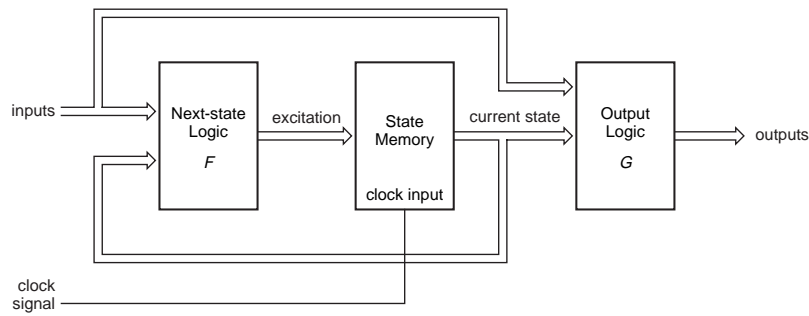

Moore:

 

Mealy machines are more powerful, but Moore machines are easier.


October 22, 2002

EE 121: Digital Design Laboratory

Lecture 8-7

Mealy machine with pipelined outputs

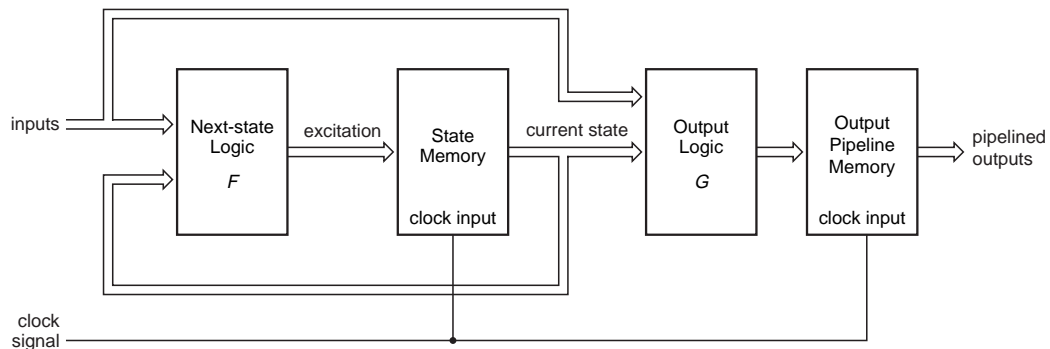Outputs of a Mealy machine can be kept constant within a clock period by using output flip-flops.



Drawback: output changes are delayed by as much as one clock cycle.

October 22, 2002

EE 121: Digital Design Laboratory

Lecture 8-8

Characteristic equations

State machine memory is built using latches or flip-flops.

Each device has a *characteristic equation* that describes how the state machine changes state as a function of the inputs.

<i>Device Type</i>	<i>Characteristic Equation</i>
S-R latch	$Q^* = S + R' \cdot Q$
D latch	$Q^* = D$
Edge-triggered D flip-flop	$Q^* = D$
D flip-flop with enable	$Q^* = EN \cdot D + EN' \cdot Q$
Master/slave S-R flip-flop	$Q^* = S + R' \cdot Q$
Master/slave J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
Edge-triggered J-K flip-flop	$Q^* = J \cdot Q' + K' \cdot Q$
T flip-flop	$Q^* = Q'$
T flip-flop with enable	$Q^* = EN \cdot Q' + EN' \cdot Q$

Table 7-1
Latch and flip-flop
characteristic
equations.

The characteristic equation of the D flip-flop is very simple, so we use it!


Clocked synchronous state machine analysis

Clocked synchronous state machines can be described in many ways:

- circuit schematic
- state and state/output tables
- transition and transition/output tables
- state diagrams (flowcharts)
- ASM (algorithmic state machine) charts
- HDL (hardware description languages)
- programming languages

A description that can be given to a CAD system for simulation and synthesis is preferred. Usually these are text descriptions, but drawing tools exist.

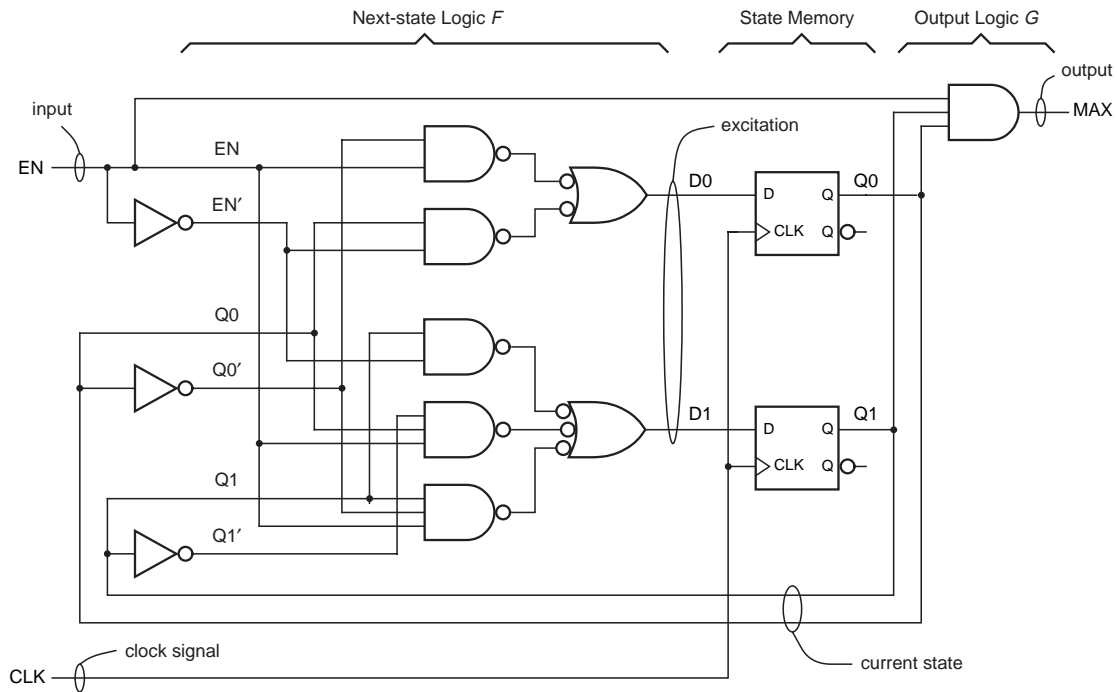Clocked synchronous state machine example



October 22, 2002

EE 121: Digital Design Laboratory

Lecture 8–11

State machine analysis

Excitation equations:

$$D0 = Q0 \cdot EN' + Q0' \cdot EN$$

$$D1 = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

Characteristic equations:

$$Q0^* = D0$$

$$Q1^* = D1$$

Transition equations:

$$Q0^* = Q0 \cdot EN' + Q0' \cdot EN$$

$$Q1^* = Q1 \cdot EN' + Q1' \cdot Q0 \cdot EN + Q1 \cdot Q0' \cdot EN$$

October 22, 2002

EE 121: Digital Design Laboratory

Lecture 8–12

Transition, state, and state/output tables

<p>(a)</p> <table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <thead> <tr> <th rowspan="2" style="border: none;">Q1 Q0</th> <th colspan="2" style="border: none;">EN</th> </tr> <tr> <th style="border: none;">0</th> <th style="border: none;">1</th> </tr> </thead> <tbody> <tr> <td style="border: none;">00</td> <td style="border: none;">00</td> <td style="border: none;">01</td> </tr> <tr> <td style="border: none;">01</td> <td style="border: none;">01</td> <td style="border: none;">10</td> </tr> <tr> <td style="border: none;">10</td> <td style="border: none;">10</td> <td style="border: none;">11</td> </tr> <tr> <td style="border: none;">11</td> <td style="border: none;">11</td> <td style="border: none;">00</td> </tr> <tr> <td style="border: none;"></td> <td style="border: none;">Q1*Q0*</td> <td style="border: none;"></td> </tr> </tbody> </table>	Q1 Q0	EN		0	1	00	00	01	01	01	10	10	10	11	11	11	00		Q1*Q0*		<p>(b)</p> <table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <thead> <tr> <th rowspan="2" style="border: none;">S</th> <th colspan="2" style="border: none;">EN</th> </tr> <tr> <th style="border: none;">0</th> <th style="border: none;">1</th> </tr> </thead> <tbody> <tr> <td style="border: none;">A</td> <td style="border: none;">A</td> <td style="border: none;">B</td> </tr> <tr> <td style="border: none;">B</td> <td style="border: none;">B</td> <td style="border: none;">C</td> </tr> <tr> <td style="border: none;">C</td> <td style="border: none;">C</td> <td style="border: none;">D</td> </tr> <tr> <td style="border: none;">D</td> <td style="border: none;">D</td> <td style="border: none;">A</td> </tr> <tr> <td style="border: none;"></td> <td style="border: none;">S*</td> <td style="border: none;"></td> </tr> </tbody> </table>	S	EN		0	1	A	A	B	B	B	C	C	C	D	D	D	A		S*		<p>(c)</p> <table border="1" style="width: 100%; border-collapse: collapse; text-align: center;"> <thead> <tr> <th rowspan="2" style="border: none;">S</th> <th colspan="2" style="border: none;">EN</th> </tr> <tr> <th style="border: none;">0</th> <th style="border: none;">1</th> </tr> </thead> <tbody> <tr> <td style="border: none;">A</td> <td style="border: none;">A, 0</td> <td style="border: none;">B, 0</td> </tr> <tr> <td style="border: none;">B</td> <td style="border: none;">B, 0</td> <td style="border: none;">C, 0</td> </tr> <tr> <td style="border: none;">C</td> <td style="border: none;">C, 0</td> <td style="border: none;">D, 0</td> </tr> <tr> <td style="border: none;">D</td> <td style="border: none;">D, 0</td> <td style="border: none;">A, 1</td> </tr> <tr> <td style="border: none;"></td> <td style="border: none;">S*, MAX</td> <td style="border: none;"></td> </tr> </tbody> </table>	S	EN		0	1	A	A, 0	B, 0	B	B, 0	C, 0	C	C, 0	D, 0	D	D, 0	A, 1		S*, MAX	
Q1 Q0		EN																																																												
	0	1																																																												
00	00	01																																																												
01	01	10																																																												
10	10	11																																																												
11	11	00																																																												
	Q1*Q0*																																																													
S	EN																																																													
	0	1																																																												
A	A	B																																																												
B	B	C																																																												
C	C	D																																																												
D	D	A																																																												
	S*																																																													
S	EN																																																													
	0	1																																																												
A	A, 0	B, 0																																																												
B	B, 0	C, 0																																																												
C	C, 0	D, 0																																																												
D	D, 0	A, 1																																																												
	S*, MAX																																																													

Table 7-2
Transition, state,
state/output table
for the state machine
in Figure 7-38.

Output equation:

$$MAX = Q1 \cdot Q0 \cdot EN$$

State diagram and timing diagram

