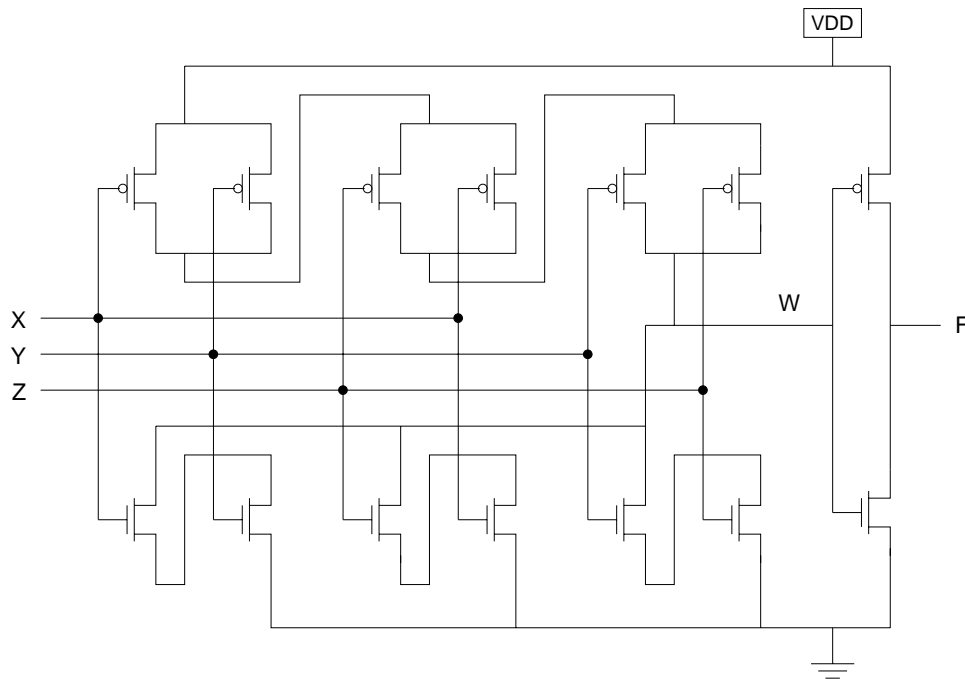


**Midterm Examination #1 Solutions**

Open book, open notes. Time limit: 75 minutes

1. (20 points) *CMOS logic circuit.* The CMOS circuit show in the figure below computes a useful logic function.



- a. Fill in the function table for the above circuit.

X	Y	Z	F
L	L	L	L
L	L	H	L
L	H	L	L
L	H	H	H
H	L	L	L
H	L	H	H
H	H	L	H
H	H	H	H

- b. Describe briefly (*not* a Boolean formula) the function computed by the above circuit.

If any two of the inputs are high, then the node W is low, so the output F is high; otherwise, F is low. In other words,  $F(X,Y,Z)$  is the majority function of three inputs.

2. (25 points) *Combinational logic.* The exclusive-or of two variables is defined to be true when one input is true but not both. Exclusive-or can be generalized to three or more variables in several ways:

XOR<sub>n</sub>Z: true if exactly one input is true.

XOR<sub>n</sub>Y: true if at least one input is true but not all inputs are true.

XOR<sub>n</sub>: true if an odd number of inputs is true.

Only the last generalization is useful; for example, XOR<sub>3</sub> is a component in a full adder.

- a. Find the minimal sum-of-products representation of XOR<sub>4</sub>Z.

It is clear from the definition of XOR<sub>n</sub>Z and from the first Karnaugh map below that XOR<sub>4</sub>Z is the sum of four minterms.

$$\text{XOR}_4Z = W \cdot X' \cdot Y' \cdot Z' + W' \cdot X \cdot Y' \cdot Z' + W' \cdot X' \cdot Y \cdot Z' + W' \cdot X' \cdot Y' \cdot Z$$

- b. Find the minimal sum-of-products representation of XOR<sub>4</sub>Y.

XOR<sub>4</sub>Y can be written as the sum of four product terms, each with two literals, in many ways. Three formulas are

$$\begin{aligned} \text{XOR}_4Y &= X \cdot Y' + W \cdot X' + W' \cdot Z + Y \cdot Z' \\ &= W' \cdot X + X \cdot Y' + W' \cdot Z + Y \cdot Z' \\ &= W \cdot Y' + Y' \cdot Z + W' \cdot Y + Y \cdot Z' \end{aligned}$$

The first expression corresponds to the covering shown in the second Karnaugh map. The second formula is obtained from the first by permuting variables. The third formula states that  $Y \neq W$  or  $Y \neq Z$ , which is sufficient to guarantee that not all input values are equal.

- c. Find the minimal product-of-sums representation of XOR<sub>4</sub>Y.

The product-of-sums representation has only two maxterms, corresponding to the two zeroes in the second Karnaugh map.

$$\begin{aligned} \text{XOR}_4Y &= (W' + X' + Y' + Z') \cdot (W + X + Y + Z) \\ &= (W \cdot X \cdot Y \cdot Z + W' \cdot X' \cdot Y' \cdot Z')' \end{aligned}$$


The second formula follows from DeMorgan's laws; only an inverter stands between sums of products and products of sums.

		WX			
		00	01	11	10
YZ	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

		WX			
		00	01	11	10
YZ	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

		WX			
		00	01	11	10
YZ	00	0	4	12	8
	01	1	5	13	9
	11	3	7	15	11
	10	2	6	14	10

 3. (30 points) *Glitches*. A devious circuit designer constructs the following circuit.




a. Find the Boolean formula for C3.

The analysis of the Boolean function computed by this circuit is extremely simple:

$$C2 = C1 \oplus C1'''' = C1 \oplus C1 = 0$$

$$C3 = C2 \oplus C2'' = C2 \oplus C2 = 0 \oplus 0 = 0$$

 b. Suppose that the propagation delay for the inverters is exactly 5 ns and the propagation delay for the XORs is exactly 10 ns. Complete the following timing diagram.



(Initial values of T1,C2,T2,C3 are not well defined because they depend on C1 for  $t < 0$ .)

c. Using the result of part (b), describe the output C3 when the input C1 is a square wave with 80 ns clock period (12.5 MHz).

C2 pulses with each transition of C1, and C3 pulses with each transition of C2. Thus C3 is a square wave with four times the frequency of C1, that is, clock period 20 ns (50 MHz)

d. Suppose that the propagation delays are given by the following table:


NOT		XOR	
$t_{\min} = 4 \text{ ns}$	$t_{\max} = 6 \text{ ns}$	$t_{\min} = 9 \text{ ns}$	$t_{\max} = 12 \text{ ns}$

Find minimum and maximum durations of the high pulses of intermediate signal C2.


Start at  $t = 10 \text{ ns}$ . To find the maximum duration of the C2 high pulse: When C1 goes high, C2 goes high in 9 ns min ( $t = 19 \text{ ns}$ ), whereas T1 will go high after 24 ns max ( $t = 34 \text{ ns}$ ). Then C2 goes back low after after 12 ns max ( $t = 46 \text{ ns}$ ). The maximum duration of the high pulse is  $46 - 19 = 27 \text{ ns}$ .

Similarly, to find the minimum duration: When C1 goes high, C2 goes high after 12 ns max ( $t = 22 \text{ ns}$ ). T1 will go high after 16 ns min ( $t = 26 \text{ ns}$ ). Then C2 goes back low after 9 ns min ( $t = 35 \text{ ns}$ ). The minimum duration of the high pulse is  $35 - 22 = 13 \text{ ns}$ .

 4. (30 points) *Funnel shifter*. An  $n$ -bit *funnel shifter* is a combinational circuit that extracts  $n$  contiguous bits from the concatenation of two  $n$ -bit words, as shown below.



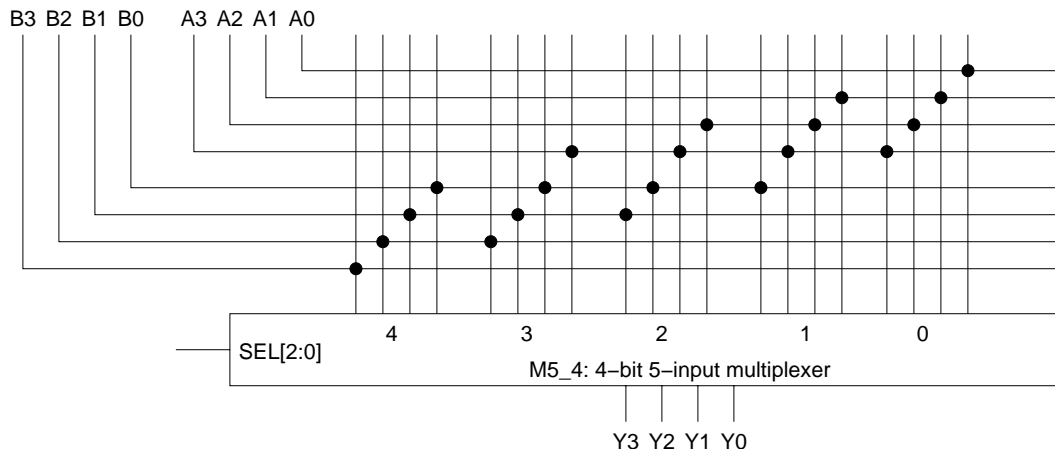- a. Complete the design of the following 4-bit funnel shifter by connecting input signals to multiplexer inputs. The *least* significant bit of the extracted field is specified by the multiplexer control inputs  $SEL[2:0]$ , as shown by the signals connected to mux input 0.



- b. A *logical left shift* SLL shifts an operand left, filling in the low-order bits with zeroes. For example,  $SLL(X[3:0], 2) = (X1, X0, 0, 0)$ . To shift an input vector  $X[3:0]$  left, the input is connected to one of the funnel shifter inputs, A or B, and zeroes are supplied to the other input. Which input is X connected to?

To perform a left shift, the data input X should be connected to the funnel shifter B inputs, which are to the “left” of the A inputs, which are connected to zeroes.

- c. What value of the control input  $SEL[2:0]$  is used to compute  $SLL(X, 3)$ ?

Shifting X left by 3 bits produces the output bit vector  $(X0, 0, 0, 0)$ , which results from the control value  $SEL[2:0] = 001 = 1$ . In general, to shift left by  $i$ , where  $0 \leq i \leq 4$ , the funnel shifter SEL input must be  $4 - i$ .

- d. A funnel shifter can also be used to *rotate* a 4-bit operand, by connecting the input operand to both data inputs of the funnel shifter. What control value  $SEL[2:0]$  is used to produce the left rotation  $ROL(X[3:0], 1) = (X2, X1, X0, X3)$ ?

To route X2 to Y3, X1 to Y2, and so on, the shift amount should be  $SEL[2:0] = 011 = 3$ . In general, to rotate left by  $i$ , where  $0 \leq i \leq 4$ , the funnel shifter SEL input must be  $4 - i$ , while to rotate right by  $i$ ,  $SEL[2:0] = i$ .