

# Lecture #9: Sequential Logic Idioms

Paul Hartke

Phartke@stanford.edu

Stanford EE121


February 7, 2002

## State Machine Design Process

1. Determination of inputs and outputs.
2. Determination of machine states.
3. Create State/Bubble Diagram—should this be a Mealy or Moore machine?
4. State Assignment—assign each state a particular value.
5. Create Transition/Output Table
6. Derive Next State Logic for each state element—using K-maps as necessary.
7. Derive Output logic.
8. Implement in Xilinx.

 
## Counters (DDPP 8.4)

- Ripple Counters gate the clock and so are **not** acceptable


 
## Synchronous Counter

- Counting is simply adding “1” to previous value.
- Use CoreGen to create Counters





## Modulo-n Counter


- If only the MSB of the Counter is considered, the counter creates a pulse every  $n$  seconds.
  - Used to create a slower periodic signal than core system clock.
  - Feed into synchronous enables to make state machines run slower
    - See Lab 5 Skeleton example.
  
## Shift Registers (DDPP 8.5)

- Used to Convert from serial data stream to parallel data stream and vice versa



## More Shift Registers

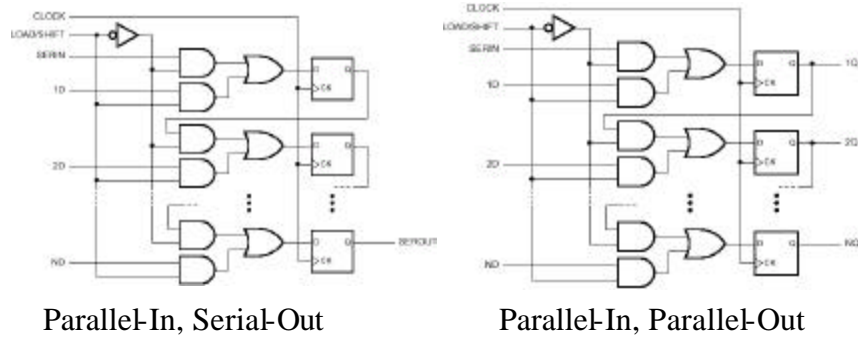


Parallel-In, Serial-Out

Parallel-In, Parallel-Out

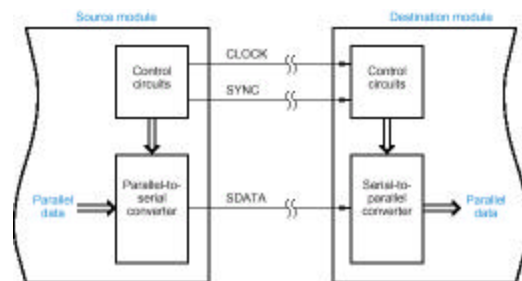
## Shift Register Applications

- Reduce Number of wires between components in a system
  - If high speed, call SerDes (Serializer, Deserializers)
  - Must make sure to synchronize signals....


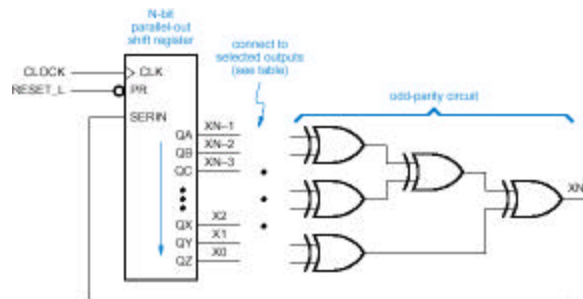
## LFSR (DDPP 8.5.8)

- Linear Feedback Shift Register
  - Non Binary Counter
  - Counts  $2^n - 1$  states



## LFSR Feedback Logic

$n$	Feedback Equation
2	$X_2 = X_1 \oplus X_0$
3	$X_3 = X_1 \oplus X_0$
4	$X_4 = X_1 \oplus X_0$
5	$X_5 = X_2 \oplus X_0$
6	$X_6 = X_1 \oplus X_0$
7	$X_7 = X_3 \oplus X_0$
8	$X_8 = X_4 \oplus X_3 \oplus X_2 \oplus X_0$
12	$X_{12} = X_6 \oplus X_4 \oplus X_1 \oplus X_0$
16	$X_{16} = X_5 \oplus X_4 \oplus X_3 \oplus X_0$
20	$X_{20} = X_3 \oplus X_0$
24	$X_{24} = X_7 \oplus X_2 \oplus X_1 \oplus X_0$
28	$X_{28} = X_3 \oplus X_0$
32	$X_{32} = X_{22} \oplus X_2 \oplus X_1 \oplus X_0$


Table 8-21  
Feedback equations  
for linear feedback  
shift-register counters.

## LFSR Applications

- LFSR's used to create pseudo-random bit sequences.
- Also, very small and compact synchronous counter.
  - Very fast
  - Why faster than binary?


## Iterative vs Sequential Circuits

- DDPP 8.6
- Space vs Time Tradeoff

 


## Serial Synchronous Circuits

- Small but long latency

 

## Another view of Decomposition

- DDPP 8.7

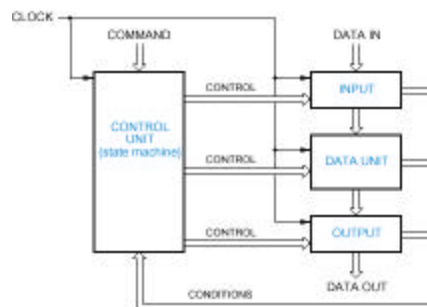

# VGA Circuit

 


Figure 1: Digital-to-analog VGA monitor interface.

# VGA Waveform

 


Figure 2: VGA signal timing.



## Lab 5 Skeleton

- VGA Document at <http://xess.com/appnotes/vga.pdf>
  - Fair game for midterm #2
- Look at in Xilinx and demo it
  - VGA Sync module
  - Character ROM
  - Registered inputs (but really should register outputs)