

# Lecture #12: The Memories..., ahh the Memories...

Paul Hartke

Phartke@stanford.edu

Stanford EE121

February 19, 2002

## Administrivia


- Make sure to fill out TA evaluations!!!
  - Incentive: 5 Point bonus on Lab 6
    - Lab 6 is only worth 60
  - Everything is anonymous
- Lab 6 Prelab is due Midnight on Thursday.
  - This allows Thursday section to have a lab section to work on the hardware.
- Reading:
  - 10.1-10.4
- Project is Assigned Today

## Memories in Digital Design

- Special Idiom in logic design.
- Different types of lookup tables (LUTs)
  - Same basic idea we have seen in the FPGA architecture.
 
## Read-Only Memory (ROM)

- Provide address and get data out
- Useful to implement complex random logic
  - Ie, Multi-bit XOR
- Really combination:




# Multiplier in ROM

**Table 10-3** Hexadecimal text file specifying the contents of a 4 × 4 multiplier ROM.

```

 00: 00 00 00 00 00 00 00 00 00 00 00 00 00 00 00
10: 00 01 02 03 04 05 06 07 08 09 0A 0B 0C 0D 0E
20: 00 02 04 06 08 0A 0C 0E 10 12 14 16 18 1A 1C
30: 00 03 06 09 0C 0F 12 15 18 1B 1E 21 24 27 2A
40: 00 04 08 0C 10 14 18 1C 20 24 28 2C 30 34 38
50: 00 05 0A 0F 14 19 1E 23 28 2D 32 37 3C 41 46
60: 00 06 0C 12 18 1E 24 2A 30 36 3C 42 48 4E 54
70: 00 07 0E 15 1C 23 2A 31 38 3F 46 4D 54 5B 62
80: 00 08 10 18 20 28 30 38 40 48 50 58 60 68 6E
90: 00 09 12 1B 24 2D 36 3F 48 51 5A 63 6C 75 7E
A0: 00 0A 14 1E 28 32 3C 46 50 5A 64 6E 78 82 8E
B0: 00 0B 16 21 2C 37 42 4D 58 63 6E 79 84 8F 93
C0: 00 0C 18 24 30 3C 48 54 60 6C 78 84 90 9C 9F
D0: 00 0D 1A 27 34 41 4E 5B 68 75 82 8F 9C A9 AB
E0: 00 0E 1C 2A 38 46 54 62 70 7E 8C 9A AB B6 B8
F0: 00 0F 1E 2D 3C 4B 5A 69 78 87 96 A5 B4 C3
    
```




# Pentium Bug—Whoops!!

- The infamous Pentium bug was caused by a ROM that was misprogrammed:
  - “The fault itself had occurred because of the omission of five entries in a table of 1,066 values (part of the chip's circuitry) used by a speedy algorithm...The five cells should have contained the constant +2, but because the cells were empty, the processor fetched a zero.”
  - [http://www.maa.org/mathland/mathland\\_5\\_12.html](http://www.maa.org/mathland/mathland_5_12.html)

 
## ROM Internal Structure

- Transistor in place indicates 1 (or vice versa depending on output polarity)



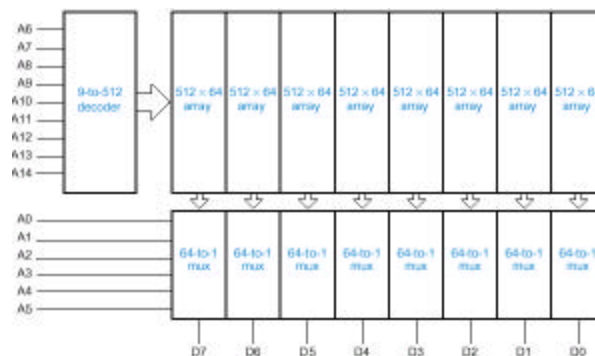
## Two-Dimensional Decoding

- Split address into row and column addressing...


 
## ROM state elements

- There are many techniques used to configure a ROM state element
  - Blow a fuse or “refill” a floating gate




## FLASH “RAM”

- Must reprogram entire sector—not random access programmable.
- Only reprogrammable a limited number of times
- The XSA-100 board has a flash on it
  - Reprogram to all 0’s and write appropriate 1’s
  - Typical 10,000 Write Cycles
- <http://www.atmel.com/atmel/acrobat/doc1008.pdf>
 
## ROM Timing


- Kind of what you might expect.
  - Chip Select and Output Enable



## Use Output Enables to Gang Parts

- Multiple parts of any memory type can be combined to make a larger system using the tristate outputs of the data bus.

## Ganging...

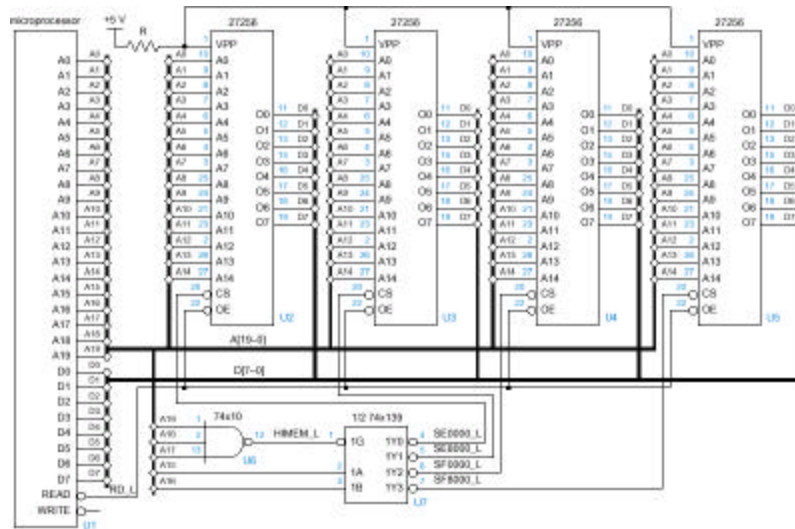


## RAM


- Static RAM (SRAM) requires no refresh cycles
  - Faster, more expensive, less dense
- Dynamic RAM (DRAM) requires a refresh cycle to keep the values current in the memory
  - Slower, less expensive, more dense
 
# SRAM

- Can now write data so need data input signals.
- Need way to indicate that a write should be performed
  - Write Enable signal



# SRAM 6T cell

 


- <http://jas2.eng.buffalo.edu/applets/education/system/memcells/sramcell/index.html>


 
## Synchronous SRAM (SSRAM)


- When flop-ed at the output called “registered”
- Helps meet board timing




## Bus Interfaces to RAM

- The turn-around penalty is involves alternating from reading to writing (& vv)
  - Requires three cycles for back-to-back read and writes.
- Delay write by providing data on next cycle.
  - Zero-Bus Turnaround (ZBT) architecture

## Regular SRAM timing

 


## ZBT Timing Diagram

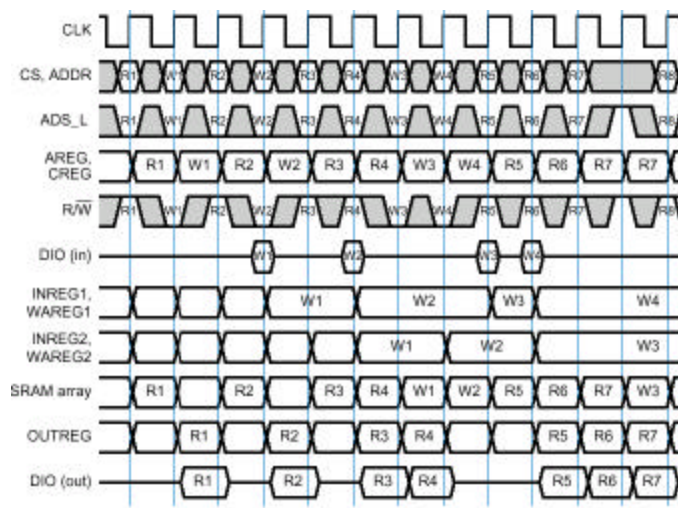

## Two Port & Dual Port

- What if you had two ports for reading and writing and accessed the same location.
  - What happens? Depends on the device
  - Old data, new data, bad data...
- If you have separate clocks then basis of circuit to pass data between clock domains...


## Xilinx Dual Port Block RAM

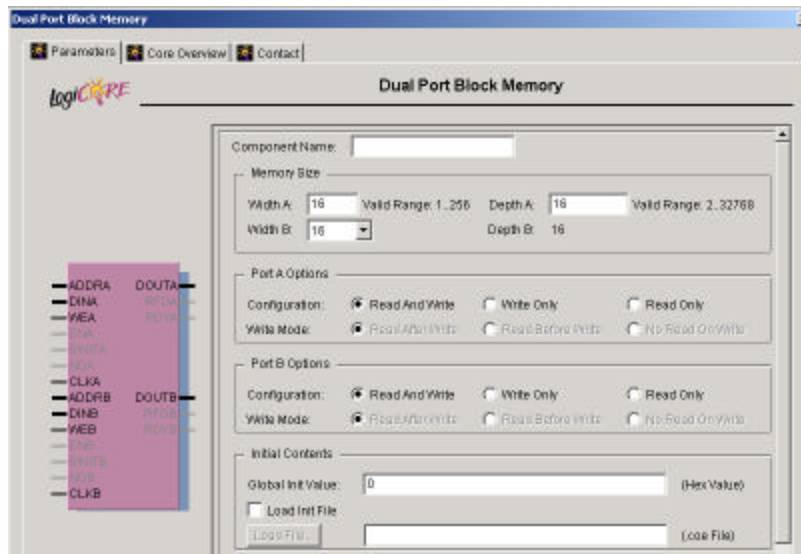


## Dynamic RAM

- SRAM like structure but present the row and column addresses separately and sense amplifier on bit lines detects output data.
- Can be Synchronous and have registered outputs.
- The one on the XSA-100 board is [http://www.hynix.co.kr/datasheet/pdf/dram/\(2\)HY57V281620A\(L\)T-L.PDF](http://www.hynix.co.kr/datasheet/pdf/dram/(2)HY57V281620A(L)T-L.PDF)

## DRAM Read Timing

 


# DRAM Write Timing

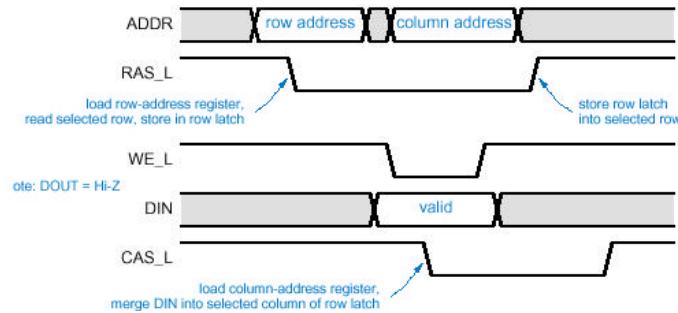

# DRAM is based on 1T cell

- Needs Refreshing every 64ms

 

- <http://jas2.eng.buffalo.edu/applets/education/system/memcells/dramcell/index.html>

## DRAM Refresh Timing



## A better DRAM cell

- “Toshiba cuts capacitor from DRAM cell design”
  - Toshiba Corp. has developed a one-transistor, no-capacitor cell structure that it claims solves the difficulties encountered in producing DRAMs in sub-0.1-micron process technology.
  - <http://www.eetimes.com/story/OEG20020207S0064>