

EE 486 lecture 9: Multiply

M. J. Flynn

Computer Architecture & Arithmetic Group
1
Stanford University


Multiply

- Generating the partial products (pp's)
 - Booth encoding
 - Direct sub multipliers
- Reducing (or assimilating) the pp's
 - Arrays (2D)
 - Higher order arrays
 - Trees (3D)
- Iteration on the pp tree (or array)

Computer Architecture & Arithmetic Group
2
Stanford University

Truncated multiply

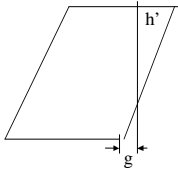- The multiplication operation forms a $2n$ bit product, but only needs to store an n bit result.
- Can truncate low order bits, if guard lsb with $g = \lceil \log_2 n \rceil$ bits plus k
- $k = 1/2 h'$ (the tree height at lsb of g)



Computer Architecture & Arithmetic Group
3
Stanford University

IEEE multiply and truncation

- In IEEE need full tree, but low order bits need only a zero detect for each bit.
- Then sticky bit, $s = \sim(\sum z_i)$ for each of the low order bits
- If we truncate $(X \times Y)^t$ then it should be that $(X \times Y)^t = (Y \times X)^t$ if non Booth is used then this is true for all X, Y since we have the same number of 1's in each column

Computer Architecture & Arithmetic Group
4
Stanford University

Truncated Booth

- This may not provide $(X \times Y)^t = (Y \times X)^t$
- Consider Booth: $2X - X$ should = X
- If $X = 00010(1)^t$
- $2X = 00101$
- $C(X^t) = 11110$ or $C(X) = 111010$,
- Not the same results

Computer Architecture & Arithmetic Group
5
Stanford University

Reducing the pp's

- The basic unit of reduction is the CSA (carry save adder)
- This is simply a binary full adder that takes 3 inputs of the same weight and provides 2 outputs, sum and carry. It's also called a (3,2) counter.
- In adding 3 numbers X, Y and Z we reduce the 3 operand to 2 and then do a single CPA

Computer Architecture & Arithmetic Group
6
Stanford University

CSAs

- By using CSAs we reduce the 3 input operands to 2 in 2 gate delays, then do a CPA
- Can extend to n operands
- In case of multiply these operands are the pp's

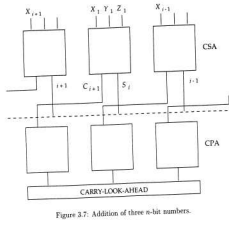


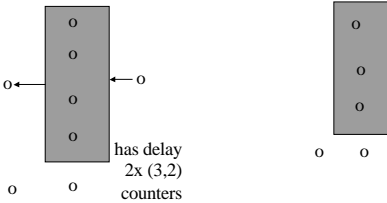


Figure 3.7: Addition of three n-bit numbers.




Computer Architecture & Arithmetic Group 7 Stanford University


Compressors and Counters

- [4:2] compressor
- (3,2) counter





has delay 2x (3,2) counters


Computer Architecture & Arithmetic Group 8 Stanford University


Multiplier topology

- Refers to the way bit positions in the pp reduction are interconnected.
- Can be either arrays or trees
- Two important measures of a topology are 1) the minimum number of wires needed to interconnect the counters within a single bit position, and 2) the number of counter delays required to reduce the pp's to the 2 inputs to the CPA.


Computer Architecture & Arithmetic Group 9 Stanford University


Using CSAs in linear arrays

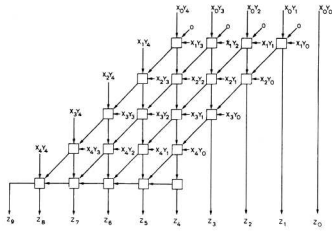






Figure 4.15: 5 x 5 unsigned multiplication.


Computer Architecture & Arithmetic Group 10 Stanford University




Linear arrays


- In a simple array each cell is a CSA
- To add n operands takes n-2 CSA levels plus a final CPA or 2(n-2) + CPA gate delays.
- While relative slow linear arrays use a minimum width of wiring channel.
- Number of wiring tracks/bit channel is w.
- w is determined by the topology. Some circuit family may require 2w to implement the design.


Computer Architecture & Arithmetic Group 11 Stanford University


Wires vs. gates

- Arrays minimize w at the expense of gate delays.
- Wiring channel can determine the column bit pitch, forcing larger designs with more overall wire.
- Some circuit techniques use 2 wires/signal (eg dual rail domino), while fast they can only be used when w can accommodate it.

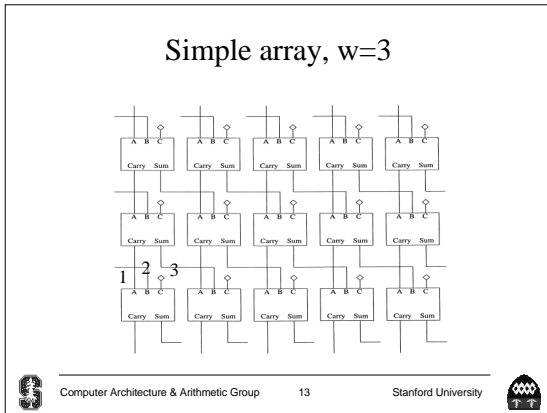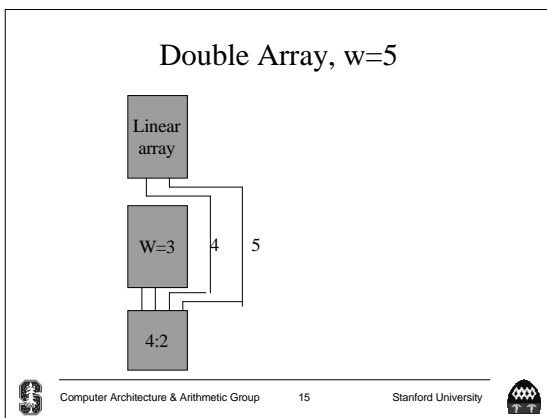

Computer Architecture & Arithmetic Group 12 Stanford University




Double arrays

- A single linear array has $w=3$ and $h=n-2$.
- A double array create 2 sub arrays of $h=(n-2)/2$; provides 4 pp's to be summed by a [4:2] and then a CPA.
- The double array has $w=5$


Computer Architecture & Arithmetic Group 14 Stanford University



Higher order arrays (Al-Twajjry'94)

- More than 2 sub arrays summed by counters or compressors.
- Optimum configurations arrange unequal length linear sub arrays into a string of [4:2] compressors so that the shortest sub array has the longest compressor chain and all paths are balanced.

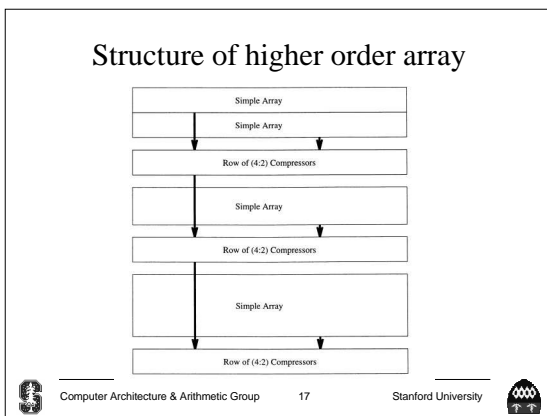Computer Architecture & Arithmetic Group 16 Stanford University



Higher order array, $w=5$

- As in the case of the double array a linear (or simple) array with $w=3$ is bypassed with the 2 outputs of a [4:2] compressor.
- Gives a total $w=5$.
- So, by construction, all arrays should have no more than $w=5$.

Computer Architecture & Arithmetic Group 18 Stanford University

Arrays, width and depth in (3,2) levels



Array type	w, lines per bit	d, # of (3,2) counters
simple	3	$n-2$
double	5	$((n-4)/2) + 2 = n/2$
higher order	5	$O(2 \sqrt{n})$

- ### Trees
- Trees differ from arrays in that they optimize depth (the number of counter delays at the expense of width, w).
 - The width of a tree (number of wires per bit position) is a function of n, the height of the pp reduction array.
 - Trees are either regular whose width is a known function of n or irregular where w is determined by design layout.

- ### Types of trees
- Wallace tree: a fast irregular tree using (3,2) counters; w depends on layout. Variations use (m,n) counters
 - Binary tree: regular tree using [4:2]s, w is predictable
 - ZM trees: regular tree with w=5 (becomes a higher order array)
 - OS (overturned staircase) trees: regular, can achieve Wallace tree delay.

Wallace ('64) big, old, trees

- The basic tree is the Wallace tree. It uses the 3,2 counter to reduce n operands to 2
- Requires about $\lceil \log_{3/2} n/2 \rceil$ levels
- No concern about w

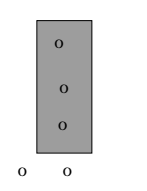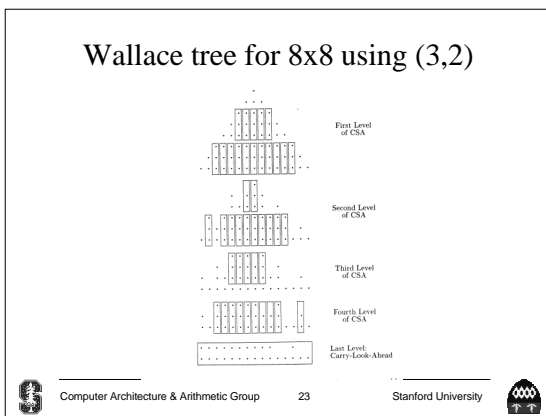Other counters can be used

- Dadda- Stenzel counters have the form (C_{R-1}, \dots, C_0, d) each C_i is the height of the ith column and d is the number of output bits
- (5,5,4) and (7,3) are the usual alternatives to (3,2)


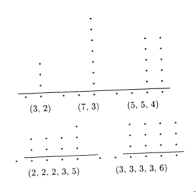


Figure 4.8: Some generalized counters from Stenzel [3]

 A 12x12 using 4x4 for pp generation and (5,5,4) counters for reduction




Counter considerations

- A ROM can be used to implement any counter: $(\sum c_i) \times d$, e.g. (2,2,2,2,2,6)
- Popular counters usually maximize the output states, so that d , almost a power of 2
- Counters are usually realized from (3,2)'s perhaps somewhat reconfigured.
- Can also have direct realizations using custom logic, PLAs tables, etc.

Compressors and counters

 - Wallace trees are irregular in structure and are difficult to layout as their wiring requirements are determined only at layout
- A more regular tree is a binary tree. This is implemented using [4:2] compressors, this is a form of (5,3) counter. It can be implemented using 2 (3,2) counters, although it's possible to reconfigure these to create a [4:2] delay faster than $2 \times (3,2)$ delays



Binary tree (Weinberger '81): 16 pp's showing 1 bit


 


Figure 4.13: Bit slice of a binary tree that reduces 16 partial products.



Binary trees

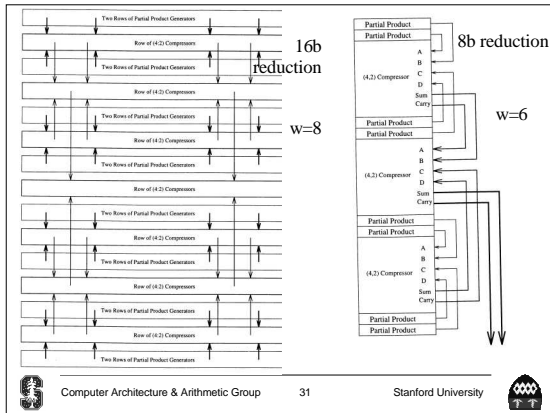- Delay in CSA levels is $2([\log_2 n] - 1)$
- Wire channel size seems to be n (the number of pp's), but it can be improved by bringing in each pp at an optimum point on the bit position of the tree.
- $w = 2[\log_2 n]$




Z M and OS trees

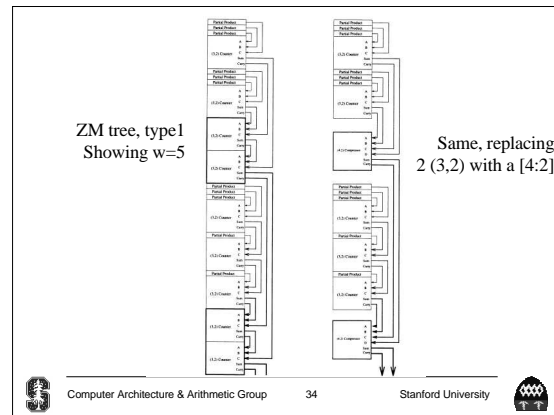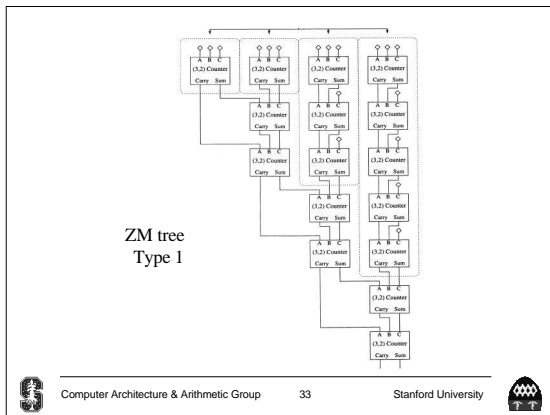- Other regular trees are possible using (3,2) or other counters
- The ZM (Zuras-McAllister '86) tree is also called a balanced delay tree. It's recursively defined by a tree body and a chain. The connection is by a [4:2]. So the tree grows as 1,1,3,5,7,... in CSA levels
- It effectively becomes a high order array with $w=5$ and $d = \Theta(2 \sqrt{n})$



Overturned staircase (OS) tree (Mou and Jutnad '90)

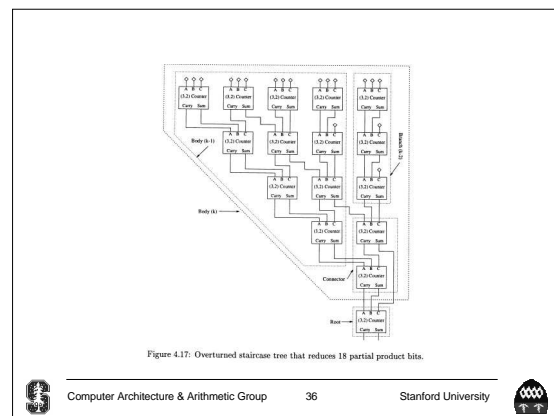- Similar to ZM but achieves Wallace tree type depth for most values of n.
- Recursively defined to connect branch of depth k-2 (CSAs) to body of depth k-1 to form tree of depth k.
- As with ZM higher order (types) are possible, with less regularity.



Multiply

- There's a broad tradeoff in topology allowing the designer to select w and d to optimize the performance of the multiplier
- Of course the pp reduction is only one part of the structure. It must be compatible with the pp generation and the CPA.

